

# Digital Design and Computer Organisation Laboratory

3rd Semester, Academic Year 2025

Date:12-08-2025

Name: Prajwal M	SRN:PES2UG24AM116	Section:B
-----------------	-------------------	-----------

Week Number: 2


Program Number: 2

TITLE:IMPLEMENTAION OF BASIC GATES IN IVERILOG

 1.

```
simple_circuit.v
1  module simple_circuit (A, B, C, D, E);
2      output D, E;
3      input A, B, C;
4      wire w1;
5
6      and G1(w1, A, B);
7      not G2(C, E);
8      or G3(w1, E, D);
9  endmodule "endmodule": Unknown word.
10
```

```
tb_simple_circuit.v
1  module tb_simple_circuit;
2
3  reg A,B,C;
4  wire D,E;
5
6  simple_circuit M1(A,B,C,D,E);
7
8  initial begin
9      #0 A=1'b0 ; B=1'b0 ; C=1'b0;
10     #20 A=1'b0 ; B=1'b0 ; C=1'b1;
11     #20 A=1'b0 ; B=1'b1 ; C=1'b0;
12     #20 A=1'b0 ; B=1'b1 ; C=1'b1;
13     #20 A=1'b1 ; B=1'b0 ; C=1'b0;
14     #20 A=1'b1 ; B=1'b0 ; C=1'b1;
15     #20 A=1'b1 ; B=1'b1 ; C=1'b0;
16     #20 A=1'b1 ; B=1'b1 ; C=1'b1;
17
18 end
19
20
21 initial begin
22     $monitor($time,"A=%b B=%b C=%b D=%b E=%b",A,B,C,D,E);
23 end
24
25 initial begin
26     $dumpfile("simple_circuit.vcd");    "dumpfile": Unknown word.
27     $dumpvars(0,tb_simple_circuit);    "dumpvars": Unknown word.
28 end
29 endmodule    "endmodule": Unknown word.
```



```
Windows PowerShell
D:\Iverlog>iverilog -o test simple_circuit.v tb_simple_circuit.v


D:\Iverlog>vvp test
VCD info: dumpfile simple_circuit.vcd opened for output.
      0A=0 B=0 C=0 D=z E=z
     20A=0 B=0 C=1 D=z E=z
     40A=0 B=1 C=0 D=z E=z
     60A=0 B=1 C=1 D=z E=z
     80A=1 B=0 C=0 D=z E=z
    100A=1 B=0 C=1 D=z E=z
    120A=1 B=1 C=0 D=z E=z
    140A=1 B=1 C=1 D=z E=z

D:\Iverlog>
```

2.

```
and2.v
1  module and2(a, b, c);
2      input a, b;
3      output c;
4      assign c = a & b;
5  endmodule "endmodule": Unknown word.
6
7  module or2(a, b, c);
8      input a, b;
9      output c;
10     assign c = a | b;
11 endmodule "endmodule": Unknown word.
12 module simple_circuit2(A, B, C, Y);
13
14     input A, B, C;
15     output Y;
16     wire w1;
17
18     and2 and2_1(B,C,w1);
19     or2 or2_1(w1,A,Y);
20
21 endmodule "endmodule": Unknown word.
```

```
tb_and2.v
1 module tb_simple_circuit;
2     reg A,B,C;
3     wire Y;
4     simple_circuit2 M1(A,B,C,Y);
5
6     initial begin
7         #0 A=1'b0 ; B=1'b0 ; C=1'b0;
8         #20 A=1'b0 ; B=1'b0 ; C=1'b1;
9         #20 A=1'b0 ; B=1'b1 ; C=1'b0;
10        #20 A=1'b0 ; B=1'b1 ; C=1'b1;
11        #20 A=1'b1 ; B=1'b0 ; C=1'b0;
12        #20 A=1'b1 ; B=1'b0 ; C=1'b1;
13        #20 A=1'b1 ; B=1'b1 ; C=1'b0;
14        #20 A=1'b1 ; B=1'b1 ; C=1'b1;
15    end
16
17    initial begin
18        $monitor($time,"A=%b B=%b C=%b Y=%b",A,B,C,Y);
19    end
20
21    initial begin
22
23        $dumpfile("simple_circuit2.vcd");    "dumpfile": Unknown word.
24        $dumpvars(0,tb_simple_circuit);    "dumpvars": Unknown word.
25    end
26 endmodule    "endmodule": Unknown word.
```

 

```
Windows PowerShell - gtkwa x + v

D:\Iverlog>iverilog -o test and2.v tb_and2.v

D:\Iverlog>vvp test
VCD info: dumpfile simple_circuit2.vcd opened for output.
      0A=0 B=0 C=0 Y=0
      20A=0 B=0 C=1 Y=0
      40A=0 B=1 C=0 Y=0
      60A=0 B=1 C=1 Y=1
      80A=1 B=0 C=0 Y=1
     100A=1 B=0 C=1 Y=1
     120A=1 B=1 C=0 Y=1
     140A=1 B=1 C=1 Y=1

D:\Iverlog>gtkwave simple_circuit2.vcd


GTKWave Analyzer v3.3.48 (w)1999-2013 BSI

[0] start time.
[140] end time.
```

### 3.

```
tb_program3.v
1  module tb_controller;
2      reg T,P,O;
3      wire F;
4
5      controller uut (T,P,O,F);
6      fan_controller uut (T,P,O,F);
7
8      initial begin
9          #10 T=0; P=0; O=0;
10         #10 T=0; P=0; O=1;
11         #10 T=0; P=1; O=0;
12         #10 T=0; P=1; O=1;
13         #10 T=1; P=0; O=0;
14         #10 T=1; P=0; O=1;
15         #10 T=1; P=1; O=0;
16         #10 T=1; P=1; O=1;
17     end
18
19     initial begin
20         $monitor($time,"T=%b P=%b O=%b F=%b",T,P,O,F);
21     end
22
23     initial begin
24         $dumpfile("tb_controller.vcd"); "dumpfile": Unknown word.
25         $dumpvars(0, tb_controller); "dumpvars": Unknown word.
26     end
27
28     endmodule "endmodule": Unknown word.
29
```

```
program3.v
1
2 module fan_controller(T, P, O, F);
3     input T,P,O;
4     output F;
5     wire TempPerson;
6
7     assign TempPerson=T&P;
8     assign F=TempPerson|O;
9
10  endmodule "endmodule": Unknown word.
11
12 module controller(T,P,O,F);
13     input T,P,O;
14     output F;
15
16     wire TempPerson;
17
18     and gate1(TempPerson, T, P);
19     or gate2(F, TempPerson, O);
20
21 endmodule "endmodule": Unknown word.
22
23
```

 

```
D:\Iverlog>iverilog -o test program3.v tb_program3.v
```

```
D:\Iverlog>vvp test
```

```
VCD info: dumpfile tb_controller.vcd opened for output.
```

```
0T=x P=x O=x F=x  
10T=0 P=0 O=0 F=0  
20T=0 P=0 O=1 F=1  
30T=0 P=1 O=0 F=0  
40T=0 P=1 O=1 F=1  
50T=1 P=0 O=0 F=0  
60T=1 P=0 O=1 F=1  
70T=1 P=1 O=0 F=1  
80T=1 P=1 O=1 F=1
```