



DIGITAL DESIGN AND COMPUTER ORGANIZATION LABORATORY

UE24CS251A

Computer Science and Engineering

Questions

1. Design and implement 2 bit up synchronous counter using JK flipflop
2. Design and implement 2 bit down synchronous counter using JK flipflop
3. Design and implement 2 bit up down synchronous counter using JK flipflop
4. Design 2 bit ripple up counter using D flipflop

Assignment:

1. Implement 3 bit ring counter using D flipflop
2. Implement 3 bit Johnson counter using D flipflop

1. Design and implement 2 bit up synchronous counter using JK flipflop


Present (Q1 Q0)	Next (Q1 ⁺ Q0 ⁺)	inputs			
		J1	K1	J0	k0
00	01	0	X	1	X
01	10	1	x	x	1
10	11	x	0	1	X
11	00	x	1	x	1

Solving using 2 variable K map of present state

J0 = 1, K0 = 1

J1 = Q0, K1 = Q0

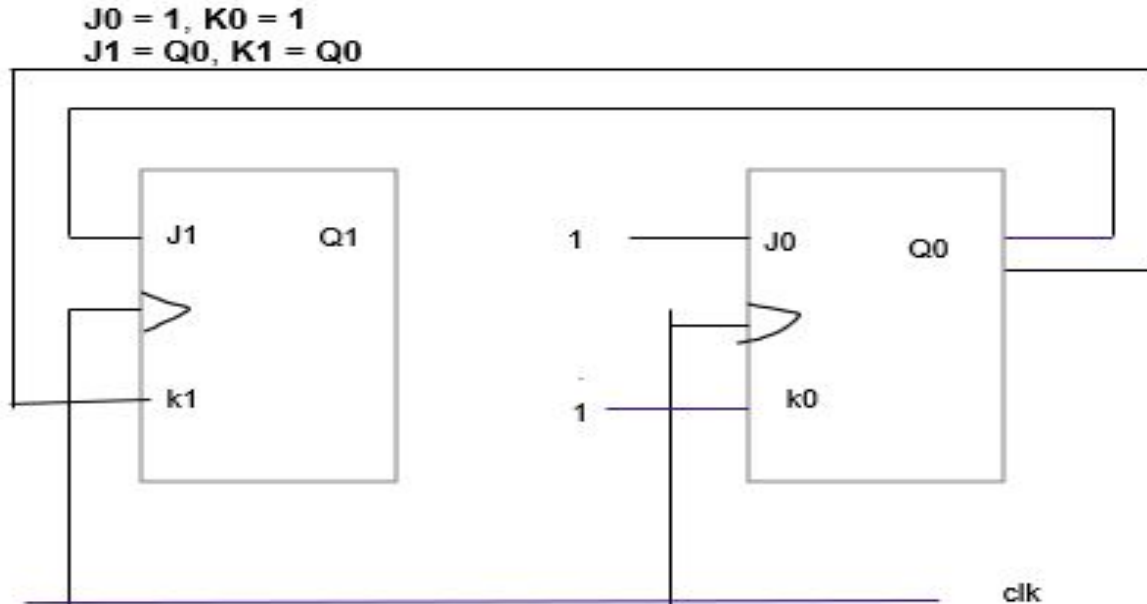Design and implement 2 bit up synchronous counter using JK flipflop



Design and implement 2 bit up synchronous counter using JK flipflop

```
Module jkff (  
// JK Flip-Flop with synchronous module  
)  
// 2-bit synchronous up counter using JK flip-flops  
module up_counter_2bit ( input clk,   input reset,   output [1:0] q);  
wire j0, k0, j1, k1;  
    assign j0 = 1'b1;  
assign K0 = 1'b1;  
assign j1 = q[0]  
    assign k1 = q[0];  
// Instantiate two JK flip-flops  
jkff jkff0 (.clk(clk), .reset(reset), .j(j0), .k(k0), .q(q[0]));  
jkff jkff1 (.clk(clk), .reset(reset), .j(j1), .k(k1), .q(q[1]));endmodule
```


2. Design and implement 2 bit Down synchronous counter using JK flipflop

Q1q0	Q1q0(next state)	J1k1	j0k0
11	10	X0	X1
10	01	X1	1x
01	00	0x	X1
00	11	1x	1x

$$J_0 = k_0 = 1$$

$$J_1 k_1 = q_0'$$

Design and implement 2 bit Down synchronous counter using JK flipflop

Define JK flipflop module

```
// 2-bit synchronous down counter using JK flip-flops
module down_counter_2bit (  input clk,  input reset,  output [1:0] q);
    // JK inputs  wire j0, k0, j1, k1;
    assign j0 ,k0 values
    assign j[1],k[1] values
    // Instantiate flip-flops
    jkff jkff0(-----);
    jkff jkff1 (-----);
endmodule
```


Design and implement 2 bit Down synchronous counter using JK flipflop-test bench

```
module tb_down_counter_2bit;
  reg clk, reset;  wire [1:0] q;
  // Instantiate counter
  down_counter_2bit uut (.clk(clk),
    .reset(reset), .q(q));
  // Clock generation
  initial begin
    clk = 0;
    forever #5 clk = ~clk; // Clock
period = 10
  end

  initial begin    $dumpfile("down_counter_jk.vcd");
    $dumpvars(0, tb_down_counter_2bit);

    $display("Time\tClk\tReset\tQ1Q0");
    $monitor("%0t\t\t%b\t\t%b\t\t%b%b", $time, clk, reset,
q[1], q[0]);

    reset = 1; #10; // Apply reset
    reset = 0;      #80; // Run counter for a while
    reset = 1; #10; // Reset again
    reset = 0;      #40;
    $finish;
  end
endmodule
```

3. Design and implement 2 bit up -Down synchronous counter using JK flipflop

M(up_dow n)-up-1, down-0	Q1q0	Q1q0 (Next state)	J1k1	j0k0
1	00	01	0x	1x
1	01	10	1x	X1
1	10	11	X0	1x
1	11	00	X1	X1
0	11	10	X0	X1
0	10	01	X1	1x
0	01	00	0x	X1
0	00	11	1x	1x

$$J_0 = k_0 = 1$$

$$J_i = k_1 = Mq_0 + M'Q_0'$$

Design and implement 2 bit up -Down synchronous counter using JK flipflop



JK flipflop module

```
module updown_counter_2bit ( input wire    clk,  input wire  
rst,  input wire    up_down, // 1: up, 0: down,  output wire  
[1:0] q);
```

Define:

J0 K0

J1 K1

// Flip-flops instantiation

Design and implement 2 bit up -Down synchronous counter using JK flipflop-test bench

```
`timescale 1ns/1ps
module tb_updown_counter_2bit;
    reg clk = 0;
    reg rst = 1;
    reg up_down = 1;
    wire [1:0] q;
    updown_counter_2bit dut (.clk(clk), .rst(rst),
    up_down(up_down), .q(q));
    // 10 ns period clock  always #5 clk = ~clk;
```

Design and implement 2 bit up -Down synchronous counter using JK flipflop-test bench

```
/ Print after each synchronous update
always @(posedge clk) begin
    $display("%0t  clk=%0b rst=%0b upDn=%0b  Q=%0b%0b",
            $time, clk, rst, up_down, q[1], q[0]);
end

initial begin
    $dumpfile("updown_2bit_jk.vcd");
    $dumpvars(0, tb_updown_counter_2bit);
```


Design and implement 2 bit up -Down synchronous counter using JK flipflop-test bench

```
// Keep reset high for one edge -> Q becomes 00 at first posedge
@(negedge clk); rst = 1;
@(negedge clk); rst = 0;    // release just before a posedge

// Count UP to reach 11: 00 -> 01 -> 10 -> 11
up_down = 1;
repeat (3) @(negedge clk);    // change only on negedge

// Now count DOWN: 11 -> 10 -> 01 -> 00
up_down = 0;
repeat (3) @(negedge clk);
$finish;
end
endmodule
```

 4. Design and implement ripple 2 bit up counter using D flipflops



4. Design and implement ripple 2 bit up counter using D flipflops

```
// Sequence: 00 → 01 → 10 → 11 → 00 → ...
`timescale 1ns/1ps
module dff (
    input wire clk,
    input wire rst, // async reset, active-high
    input wire d,
    output reg q
);
    always @(posedge clk or posedge rst) begin
        if (rst) q <= 1'b0;
        else    q <= d;
    end
endmodule
```


4. Design and implement ripple 2 bit up counter using D flipflops

```
module ripple_up_counter_2bit (  
    input wire clk,  
    input wire rst,  
    output wire [1:0] q  
);  
    wire q0, q1;  
    // LSB toggles every system clock  
    dff ff0 (.clk(clk), .rst(rst), .d(~q0), .q(q0));  
  
    // MSB toggles when q0 falls (use posedge of ~q0)  
    dff ff1 (.clk(~q0), .rst(rst), .d(~q1), .q(q1));  
    assign q = {q1, q0};  
endmodule
```

Thank you