

Digital Design and Computer Organisation Laboratory

3rd Semester, Academic Year 2025

Date:19-08-2025

Name: Prajwal M	SRN:PES2UG24CS910	Section:C
-----------------	-------------------	-----------

Week Number: 3

Program Number: 3

TITLE:IMPLEMENTAION OF HALF,FULL,RIPPLE CARRY ADDER

1.HALF ADDER

```
halfadd.v
1 module halfadd(a, b,sum, cout); "halfadd": Unknown word.
2 input a, b;
3 output sum, cout; "cout": Unknown word.
4 xor2 x0(a,b,sum);
5 and2 a0(a,b,cout); "cout": Unknown word.
6 endmodule "endmodule": Unknown word.
7
```

```

1  module halfadd_tb;    "halfadd": Unknown word.
2  reg aa,bb;
3  wire ss,cy;
4  halfadd add1(.a(aa), .b(bb), .sum(ss), .cout(cy));    "halfadd": Unknown word.
5  initial
6  begin
7  $dumpfile("halfadd_test.vcd");    "dumpfile": Unknown word.
8  $dumpvars(0, halfadd_tb);    "dumpvars": Unknown word.
9  end
10
11 initial
12 begin
13 $monitor($time, "a=%b, b=%b, sum=%b, carry=%b", aa, bb, ss, cy);
14 aa = 1'b0;bb = 1'b0;
15 #5 aa = 1'b0;bb = 1'b1;
16 #5 aa = 1'b1;bb = 1'b0;
17 #5 aa = 1'b1;bb = 1'b1;
18 end
19 endmodule    "endmodule": Unknown word.
20

```

```
D:\iverilog lab\week 3>iverilog -o halfadd halfadd.v basic.v halfadder_tb.v
```

```
D:\iverilog lab\week 3>vvp halfadd
```

```
VCD info: dumpfile halfadd_test.vcd opened for output.
```


```
0a=0, b=0, sum=0, carry=0
```

```
5a=0, b=1, sum=1, carry=0
```

```
10a=1, b=0, sum=1, carry=0
```

```
15a=1, b=1, sum=0, carry=1
```

```
D:\iverilog lab\week 3>
```

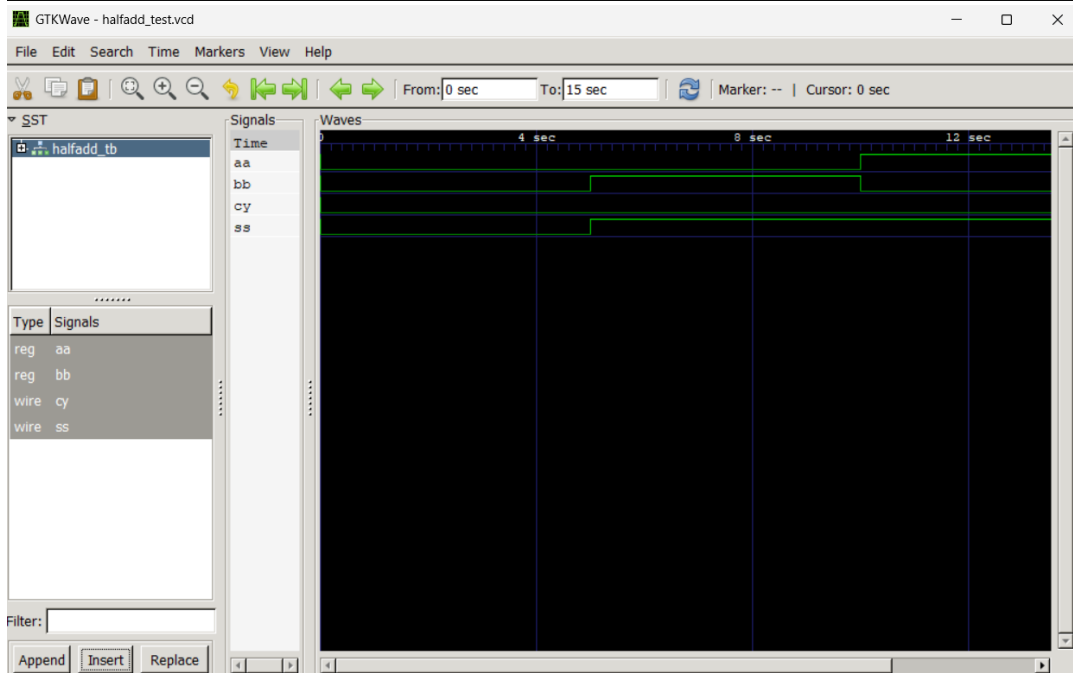

2.FULL ADDER

```
fulladder.v
1 module fulladder(a, b, cin, sum, cout); "fulladder": Unknown word.
2     input a, b, cin;
3     output sum, cout; "cout": Unknown word.
4     wire w1, w2, w3, w4, w5;
5
6     xor2 x1(a, b, w1);
7     xor2 x2(w1, cin, sum);
8
9     and2 a1(a, b, w2);
10    and2 a2(b, cin, w3);
11    and2 a3(a, cin, w4);
12    or2 o1(w2, w3, w5);
13    or2 o2(w5, w4, cout); "cout": Unknown word.
14 endmodule "endmodule": Unknown word.
15
```

```
fulladder_tb.v
1 module fulladder_tb; "fulladder": Unknown word.
2     reg aa, bb, cc;
3     wire ss, cy;
4
5     fulladder uut(.a(aa),.b(bb),.cin(cc),.sum(ss),.cout(cy)); "fulladder": Unknown word.
6
7     initial begin
8         $dumpfile("fulladder_test.vcd"); "dumpfile": Unknown word.
9         $dumpvars(0, fulladder_tb); "dumpvars": Unknown word.
10    end
11
12    initial begin
13        $monitor($time, "a=%b, b=%b, cin=%b, sum=%b, cout=%b", aa, bb, cc, ss, cy); "cout": Unknown word.
14        #5 aa=1'b0; bb=1'b0; cc=1'b0;
15        #5 aa=1'b0; bb=1'b1; cc=1'b0;
16        #5 aa=1'b1; bb=1'b0; cc=1'b0;
17        #5 aa=1'b1; bb=1'b1; cc=1'b0;
18        #5 aa=1'b0; bb=1'b0; cc=1'b1;
19        #5 aa=1'b0; bb=1'b1; cc=1'b1;
20        #5 aa=1'b1; bb=1'b0; cc=1'b1;
21        #5 aa=1'b1; bb=1'b1; cc=1'b1;
22        $finish;
23    end
24 endmodule "endmodule": Unknown word.
25
```


```

D:\iverilog lab\week 3>iverilog -o fulladd fulladder.v basic.v halfadd.v fulladder_tb.v

D:\iverilog lab\week 3>vvp fulladd
VCD info: dumpfile fulladder_test.vcd opened for output.
      0a=x, b=x, cin=x, sum=x, cout=x
      5a=0, b=0, cin=0, sum=0, cout=0
     10a=0, b=1, cin=0, sum=1, cout=0
     15a=1, b=0, cin=0, sum=1, cout=0
     20a=1, b=1, cin=0, sum=0, cout=1
     25a=0, b=0, cin=1, sum=1, cout=0
     30a=0, b=1, cin=1, sum=0, cout=1
     35a=1, b=0, cin=1, sum=0, cout=1
     40a=1, b=1, cin=1, sum=1, cout=1

D:\iverilog lab\week 3>

```

 

3.RIPPLE CARRY ADDER

```

1 module ripple_carry_adder(input wire [3:0] a, b, input wire cin, output wire [3:0] sum, output wire cout);    "cout": Unknown word.
2     wire [2:0] c;
3     fulladder u0 (.a(a[0]), .b(b[0]), .cin(cin), .sum(sum[0]), .cout(c[0]));    "fulladder": Unknown word.
4     fulladder u1 (.a(a[1]), .b(b[1]), .cin(c[0]), .sum(sum[1]), .cout(c[1]));    "fulladder": Unknown word.
5     fulladder u2 (.a(a[2]), .b(b[2]), .cin(c[1]), .sum(sum[2]), .cout(c[2]));    "fulladder": Unknown word.
6     fulladder u3 (.a(a[3]), .b(b[3]), .cin(c[2]), .sum(sum[3]), .cout(cout));    "fulladder": Unknown word.
7     endmodule    "endmodule": Unknown word.
8

```

```

1 timescale 1 ns / 100 ps
2 `define TESTVECS 10 "TESTVECS": Unknown word.
3 module tb;
4 reg clk, reset;
5 reg [3:0] i0, i1;
6 reg cin;
7 wire [3:0] o;
8 wire cout; "cout": Unknown word.
9 reg [8:0] test_vecs [0:('TESTVECS-1)]; "vecs": Unknown word.
10 integer i;
11 initial
12 begin
13 $dumpfile("rca_test.vcd"); "dumpfile": Unknown word.
14 $dumpvars(0,tb); "dumpvars": Unknown word.
15 end
16
17 initial
18 begin
19 reset = 1'b1; #12.5 reset = 1'b0; end initial clk = 1'b0; always #5 clk =~ clk;
20 initial begin
21 test_vecs[0] = 9'b00000000; "vecs": Unknown word.
22 test_vecs[1] = 9'b00000001; "vecs": Unknown word.
23 test_vecs[2] = 9'b00010001; "vecs": Unknown word.
24 test_vecs[3] = 9'b00010011; "vecs": Unknown word.
25 test_vecs[4] = 9'b00100010; "vecs": Unknown word.
26 test_vecs[5] = 9'b00100011; "vecs": Unknown word.
27 test_vecs[6] = 9'b10101010; "vecs": Unknown word.
28 test_vecs[7] = 9'b10101011; "vecs": Unknown word.
29 test_vecs[8] = 9'b11101110; "vecs": Unknown word.
30 test_vecs[9] = 9'b11101111; "vecs": Unknown word.
31 end
32
33
34 initial {i0, i1, cin, i} = 0;
35 ripple_carry_adder u0 (i0, i1, cin, o, cout); "cout": Unknown word.
36 initial begin #6
37 for(i=0;i<'TESTVECS;i=i+1) "TESTVECS": Unknown word.
38 begin #10 {i0, i1, cin}=test_vecs[i]; "vecs": Unknown word.
39 end #100 $finish; end
40 always@(i0 or i1 or cin)
41 $monitor("At time = %t, i0=%b, i1=%b,cin=%b,Sum = %b,Carry %b", $time,i0,i1,cin,o,cout); "cout": Unknown word.
42 endmodule "endmodule": Unknown word.
43

```

```

Windows PowerShell
D:\iverilog lab\week 3>iverilog -o rippadd fulladder.v basic.v ripple_carry_adder.v ripple_carry_adder_tb.v

D:\iverilog lab\week 3>vvp rippadd
VCD info: dumpfile rca_test.vcd opened for output.
At time = 0, i0=0000, i1=0000,cin=0,Sum = 0000,Carry 0
At time = 260, i0=0000, i1=0000,cin=1,Sum = 0001,Carry 0
At time = 360, i0=0001, i1=0001,cin=0,Sum = 0010,Carry 0
At time = 460, i0=0001, i1=0001,cin=1,Sum = 0011,Carry 0
At time = 560, i0=0010, i1=0010,cin=0,Sum = 0100,Carry 0
At time = 660, i0=0010, i1=0010,cin=1,Sum = 0101,Carry 0
At time = 760, i0=1010, i1=1011,cin=0,Sum = 0101,Carry 1
At time = 860, i0=1010, i1=1011,cin=1,Sum = 0110,Carry 1
At time = 960, i0=1110, i1=1111,cin=0,Sum = 1101,Carry 1
At time = 1060, i0=1110, i1=1111,cin=1,Sum = 1110,Carry 1

D:\iverilog lab\week 3>

```

